

**EE414 Embedded Systems**

**Ch 2. Custom Single-  
Purpose Processors:  
Hardware**



Byung Kook Kim  
School of Electrical Engineering  
Korea Advanced Institute of Science and Technology

# Outline

---

- 2.1 Introduction

## **Review Digital Logic**

- 2.2 Combinational logic
- 2.3 Sequential logic

## **Custom Single-Purpose Processor**

- 2.4 Custom single-purpose processor design
- 2.5 RT-level custom single-purpose processor design
- 2.6 Optimizing custom single-purpose processors


# 2.1 Introduction

## ■ Processor

- Digital circuit that performs computation tasks
- Controller and datapath
- General-purpose: variety of computation tasks
- Single-purpose: one particular computation task
- Custom single-purpose processor: non-standard task
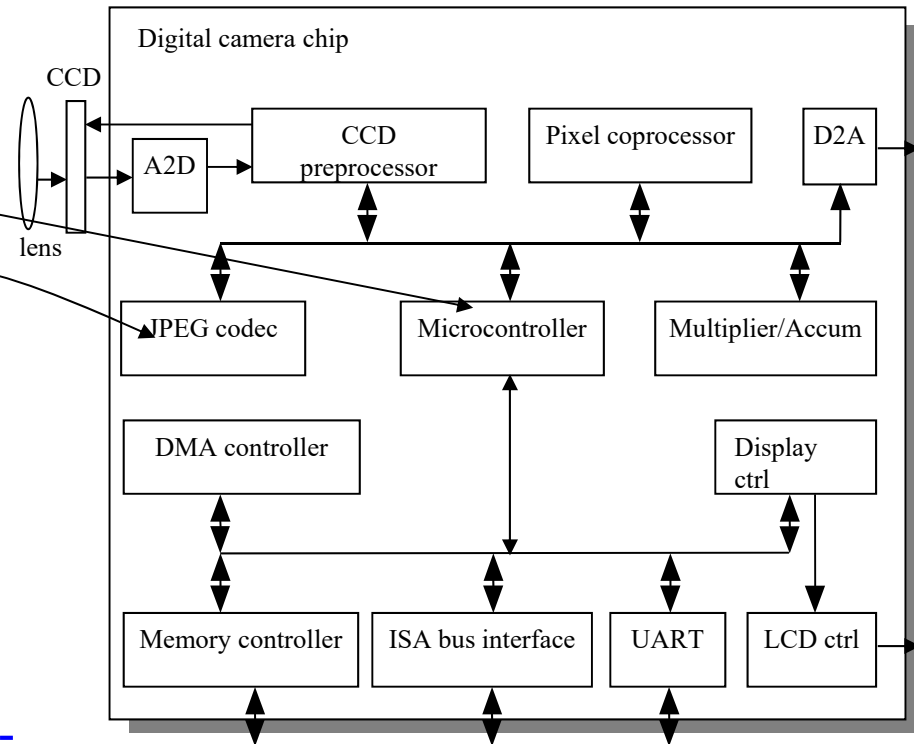
## ■ Custom single-purpose processor

- Faster, smaller, low power
- But, high NRE cost, longer time-to-market, less flexible.




# 2.2 Combinational Logic

## Transistors and Logic Gates
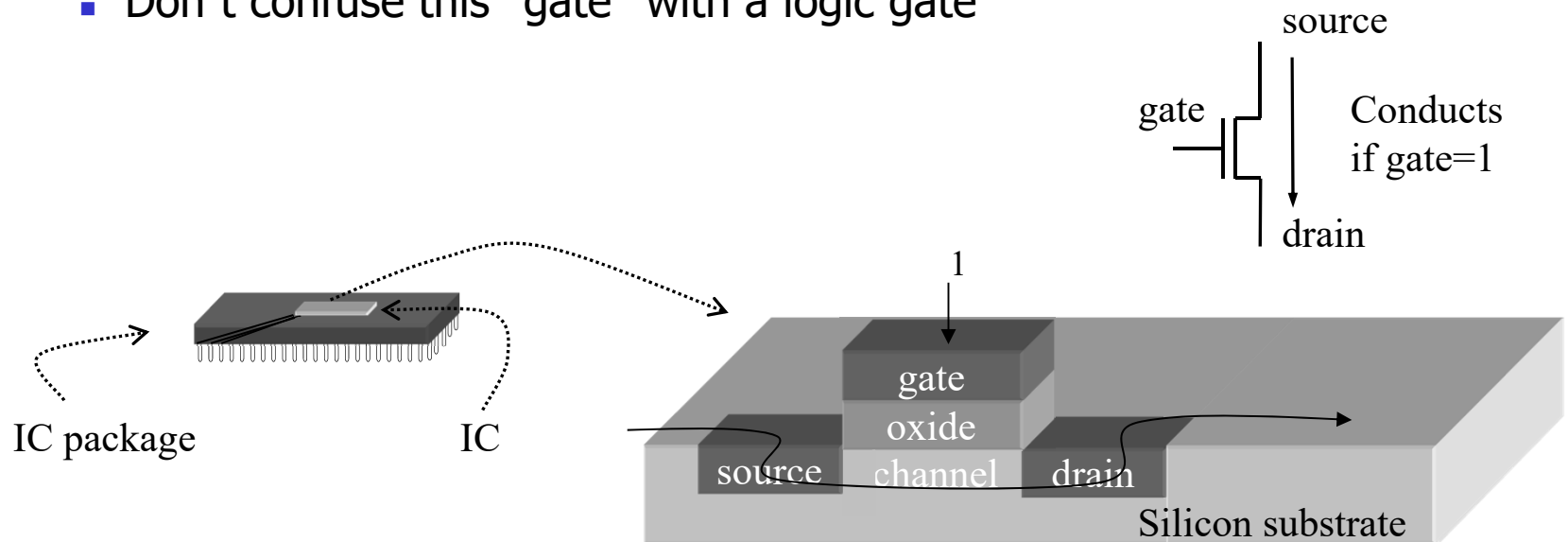
### ■ Transistor

- The basic electrical component in digital systems.
- Acts as an **on/off switch** (not as an amplifier).
- **Voltage at “gate” controls** whether current flows from source to drain
  - Don't confuse this “gate” with a logic gate



# CMOS transistor – Logic gate implementations


- **CMOS: Complementary Metal Oxide Semiconductor**
  - Most widely used. Transistor < Logic gates < Digital systems.

- We refer to logic levels

- Typically 0 is 0V, 1 is 5V


- Two basic CMOS TR types

 - nMOS conducts if gate=1 →
- pMOS conducts if gate=0 →
- Hence “complementary”




- **Basic logic gates**

- Inverter, NAND, NOR →

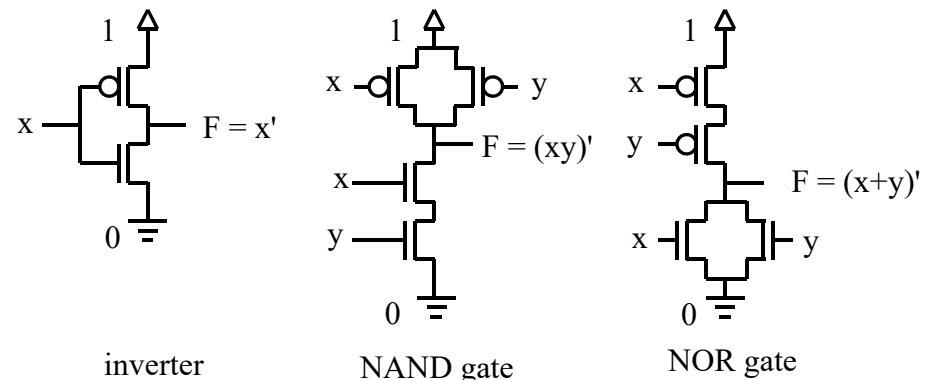


# Basic Logic Gates

 


x	F
0	0
1	1

$F = x$   
Driver

 


x	y	F
0	0	0
0	1	0
1	0	0
1	1	1

$F = x y$   
AND

 


x	y	F
0	0	0
0	1	1
1	0	1
1	1	1

$F = x + y$   
OR

 


x	y	F
0	0	0
0	1	1
1	0	1
1	1	0

$F = x \oplus y$   
XOR

 


x	F
0	1
1	0

$F = x'$   
Inverter

 


x	y	F
0	0	1
0	1	1
1	0	1
1	1	0

$F = (x y)'$   
NAND

 

x	y	F
0	0	1
0	1	0
1	0	0
1	1	0

$F = (x+y)'$   
NOR

 

x	y	F
0	0	1
0	1	0
1	0	0
1	1	1

$F = x \odot y$   
XNOR

- Digital system designers usually work at the abstraction level of **logic gates** rather than **transistors**.
- Transistor < Logic gates < Digital systems.

# Basic Combinational Logic Design

Combinational circuit: Output purely function of present input (No memory)

## A) Problem description

**y is 1 if a is to 1, or b and c are 1. z is 1 if b or c is to 1, but not both, or if all are 1.**

## B) Truth table

Inputs			Outputs	
a	b	c	y	z
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

## C) Output equations

$$y = a'bc + ab'c' + ab'c + abc' + abc$$

$$z = a'b'c + a'bc' + ab'c + abc' + abc$$

## D) Minimized output equations

y	bc			
a	00	01	11	10
0	0	0	1	0
1	1	1	1	1


$$y = a + bc$$

z	bc			
a	00	01	11	10
0	0	1	0	1
1	0	1	1	1

$$z = ab + b'c + bc'$$

**Karnaugh maps:**  
Maximize squares enclosing 1's.

## E) Logic Gates

 

# RT-level combinational components

## Multiplexer, Decoder, Adder, Comparator, and ALU

<p> <math>O =</math>  <math>I_0</math> if <math>S=0..00</math>  <math>I_1</math> if <math>S=0..01</math>  <math>\dots</math>  <math>I_{(m-1)}</math> if <math>S=1..11</math> </p>	<p> <math>O_0 = 1</math> if <math>I=0..00</math>  <math>O_1 = 1</math> if <math>I=0..01</math>  <math>\dots</math>  <math>O_{(n-1)} = 1</math> if <math>I=1..11</math> </p>	<p> <math>sum = A+B</math>                      (first <math>n</math> bits)  <math>carry = (n+1)</math>'th                      bit of <math>A+B</math> </p>	<p> <math>less = 1</math> if <math>A &lt; B</math>  <math>equal = 1</math> if <math>A = B</math>  <math>greater = 1</math> if <math>A &gt; B</math> </p>	<p> <math>O = A \text{ op } B</math>  <math>op</math> determined                      by <math>S</math>.                 </p>
	<p>With enable input <math>e \rightarrow</math> all <math>O</math>'s are 0 if <math>e=0</math></p>	<p>With carry-in input <math>C_i \rightarrow</math> <math>sum = A + B + C_i</math></p>		<p>May have status outputs carry, zero, etc.</p>



# 2.3 Sequential Logic




---

## Flip-Flops

- **Sequential circuit**
  - A digital circuit whose outputs are function of the present as well as previous input values
  - Sequential logic possesses **memory**: Combinational logic and memory.
  - Ex. Coffee vending machine
- **Flip-flop**
  - Basic memory in sequential circuit
  - D flip-flop
  - SR flip-flop
  - JK flip-flop
  - Level triggered
  - Edge triggered

# RT-level sequential components

- Register, shift register, and counter

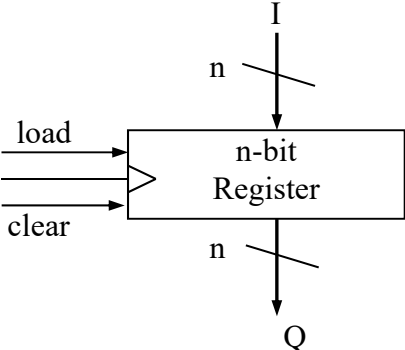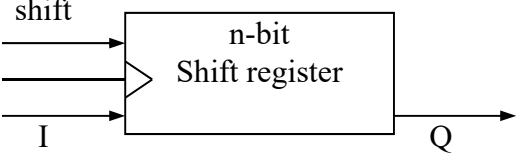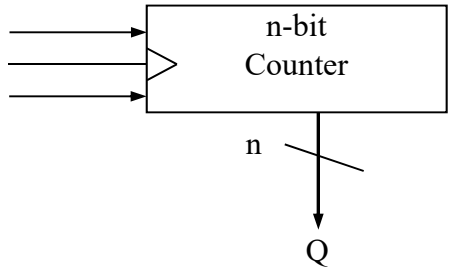		
<p>Q =            0 if clear=1,            I if load=1 and clock=1,            Q(previous) otherwise.</p>	<p>Q = lsb            - Content shifted            - I stored in msb</p>	<p>Q =            0 if clear=1,            Q(prev)+1 if count=1 and            clock=1.</p>


- Synchronous:** Input value has an affect during clock edge.
- Asynchronous:** Input value affects the circuit independent of clock.

# Sequential Logic Design


## A) Problem Description

You want to construct a clock divider. Slow down your pre-existing clock so that you output a 1 for every four clock cycles

## B) State Diagram

 

## C) Implementation Model


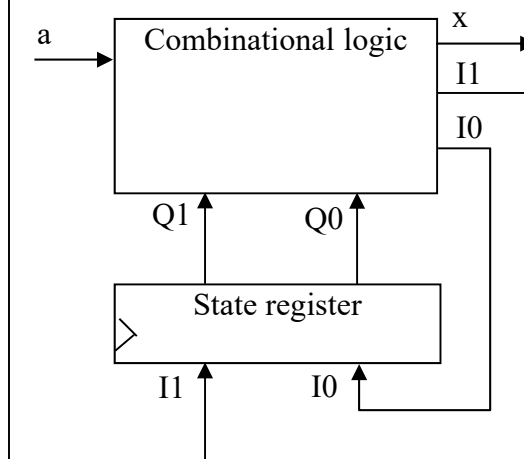


## D) State Table (Moore-type)

Inputs			Outputs		
Q1	Q0	a	I1	I0	x
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	1


- State diagram
  - Finite State Machine (FSM)
- Given this implementation model
  - Sequential logic design quickly reduces to combinational logic design.

# Sequential logic design (cont.)

 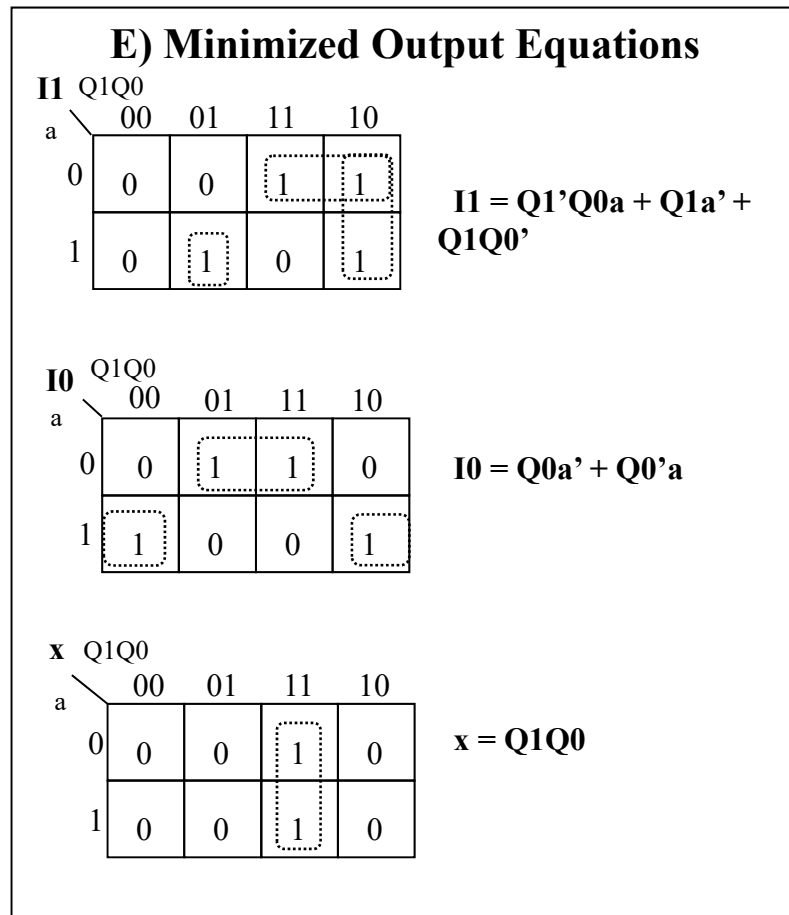

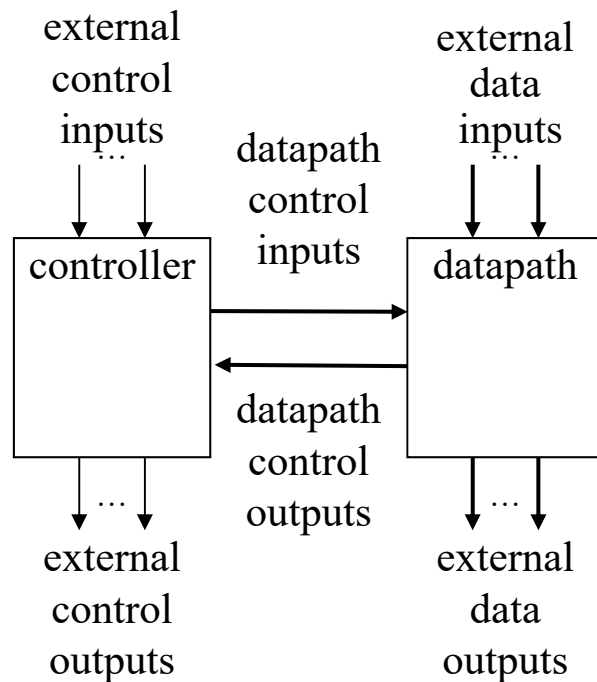
# 2.4 Custom Single-Purpose Processor Design

- A basic processor model
  - Controller: Control datapath.
  - Datapath: Manipulate and store.



## Controller and datapath


- Inside view

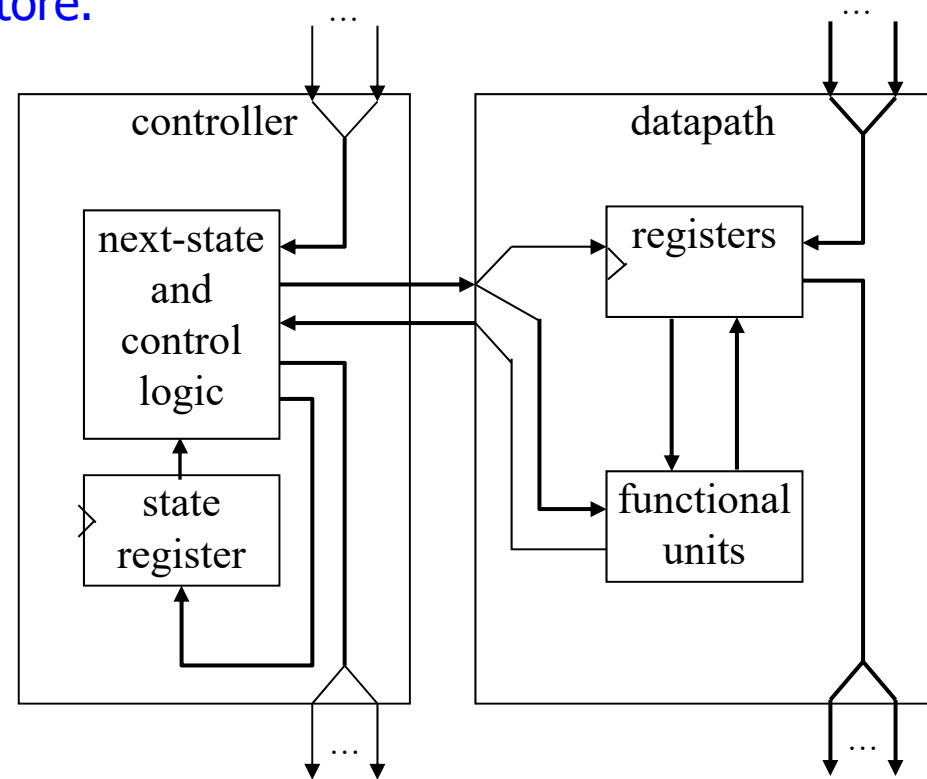

A view inside the controller and datapath

# Design example: Greatest Common Divisor

 
- 1. First create **algorithm**
  - Subtraction (b)
- 2. Convert algorithm to “**complex**” state machine (c)
  - Known as **FSMD**:  
finite-state machine with data
  - Can use **templates** to perform such conversion



(b) desired functionality

```

 0: int x, y;
1: while (1) {
2:   while (!go_i);
3:   x = x_i;
4:   y = y_i;
5:   while (x != y) {
6:     if (x < y)
7:       y = y - x;
8:     else
9:       x = x - y;
9:   }
9:   d_o = x;
}
  
```




# 2. State diagram templates

## Templates

### ■ (a) Assignment

Assignment statement


```
a = b
next statement
```

 
 
### (b) Loop

Loop statement


```
while (cond) {
    loop-body-
    statements
}
next statement
```


 
### (c) Branch


Branch statement

```
if (c1)
    c1 stmts
else if c2
    c2 stmts
else
    other stmts
next statement
```




# 3. Creating the datapath

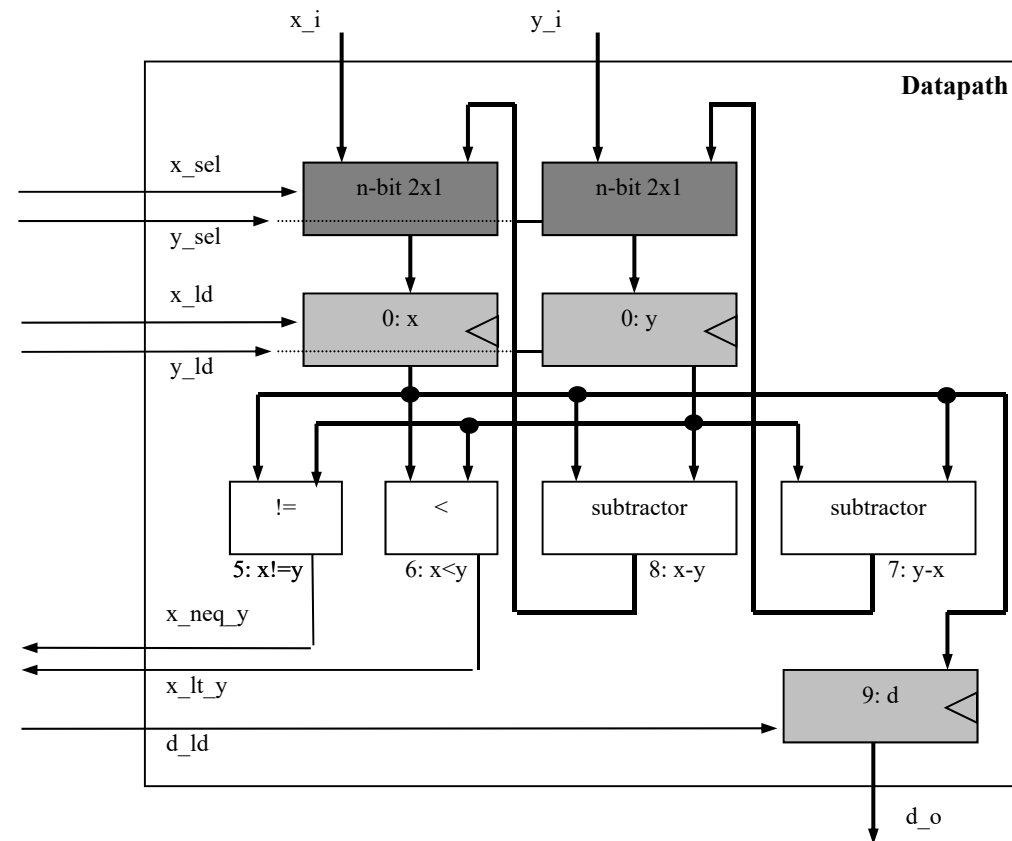- 1. Create a **register** & **ports** for any declared variable
- 2. Create a **functional unit** for each arithmetic operation
- 3. **Connect** the ports, registers and functional units
  - Based on reads and writes
  - Use **multiplexers** for multiple sources
- 4. Create **unique identifier**
  - for each datapath component control input and output





# 4. Creating the controller's FSM

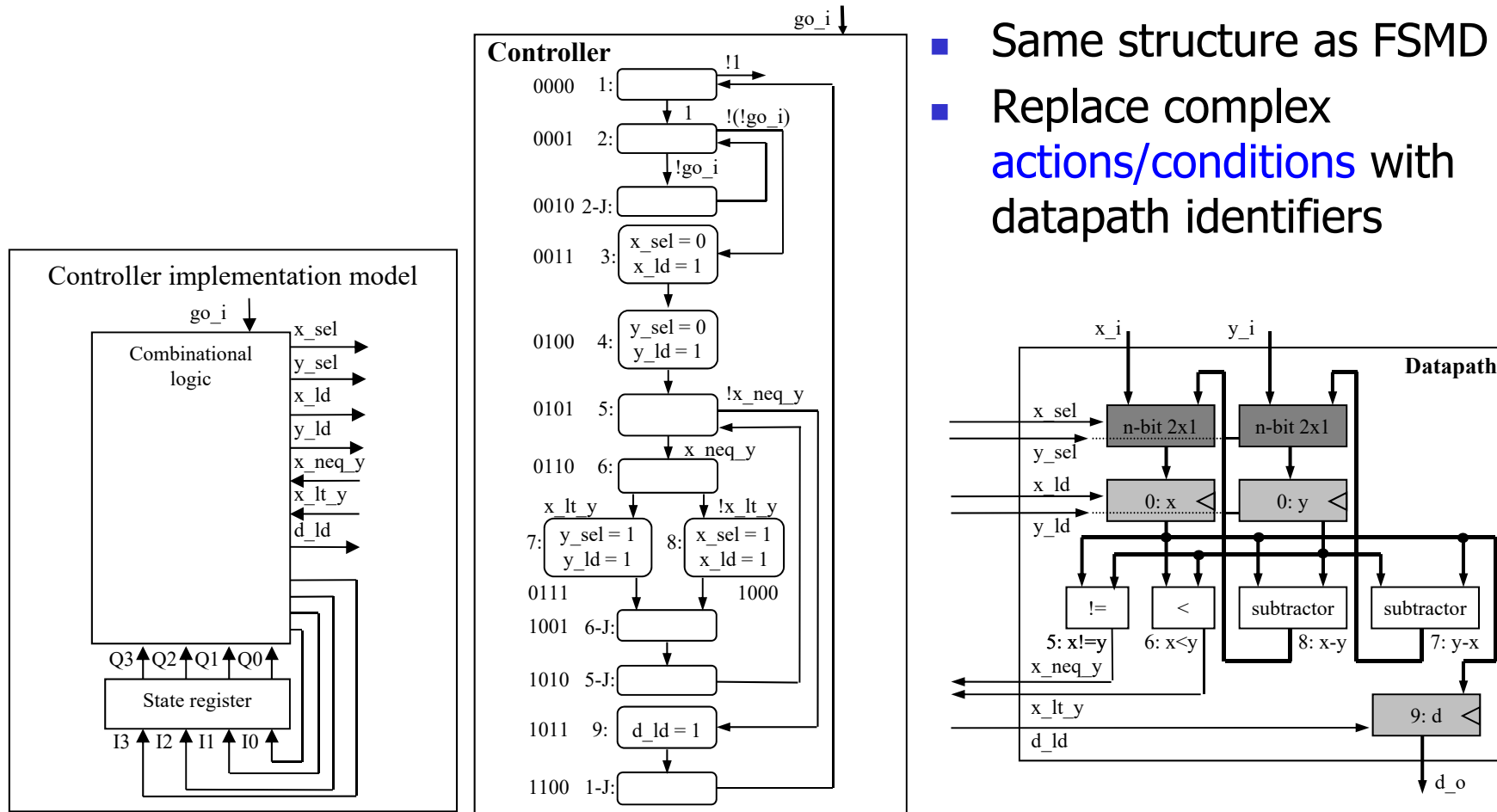


- Same structure as FSMD
- Replace complex actions/conditions with datapath identifiers

# 5. Controller state table for the GCD example

Inputs							Outputs									
Q3	Q2	Q1	Q0	x_neq_y	x_lt_y	go_i	I3	I2	I1	I0	x_sel	y_sel	x_ld	y_ld	d_ld	
0	0	0	0	*	*	*	0	0	0	1	X	X	0	0	0	
0	0	0	1	*	*	0	0	0	1	0	X	X	0	0	0	
0	0	0	1	*	*	1	0	0	1	1	X	X	0	0	0	
0	0	1	0	*	*	*	0	0	0	1	X	X	0	0	0	
0	0	1	1	*	*	*	0	1	0	0	0	X	1	0	0	
0	1	0	0	*	*	*	0	1	0	1	X	0	0	1	0	
0	1	0	1	0	*	*	1	0	1	1	X	X	0	0	0	
0	1	0	1	1	*	*	0	1	1	0	X	X	0	0	0	
0	1	1	0	*	0	*	1	0	0	0	X	X	0	0	0	
0	1	1	0	*	1	*	0	1	1	1	X	X	0	0	0	
0	1	1	1	*	*	*	1	0	0	1	X	1	0	1	0	
1	0	0	0	*	*	*	1	0	0	1	1	X	1	0	0	
1	0	0	1	*	*	*	1	0	1	0	X	X	0	0	0	
1	0	1	0	*	*	*	0	1	0	1	X	X	0	0	0	
1	0	1	1	*	*	*	1	1	0	0	X	X	0	0	1	
1	1	0	0	*	*	*	0	0	0	0	X	X	0	0	0	
1	1	0	1	*	*	*	0	0	0	0	X	X	0	0	0	
1	1	1	0	*	*	*	0	0	0	0	X	X	0	0	0	
1	1	1	1	*	*	*	0	0	0	0	X	X	0	0	0	
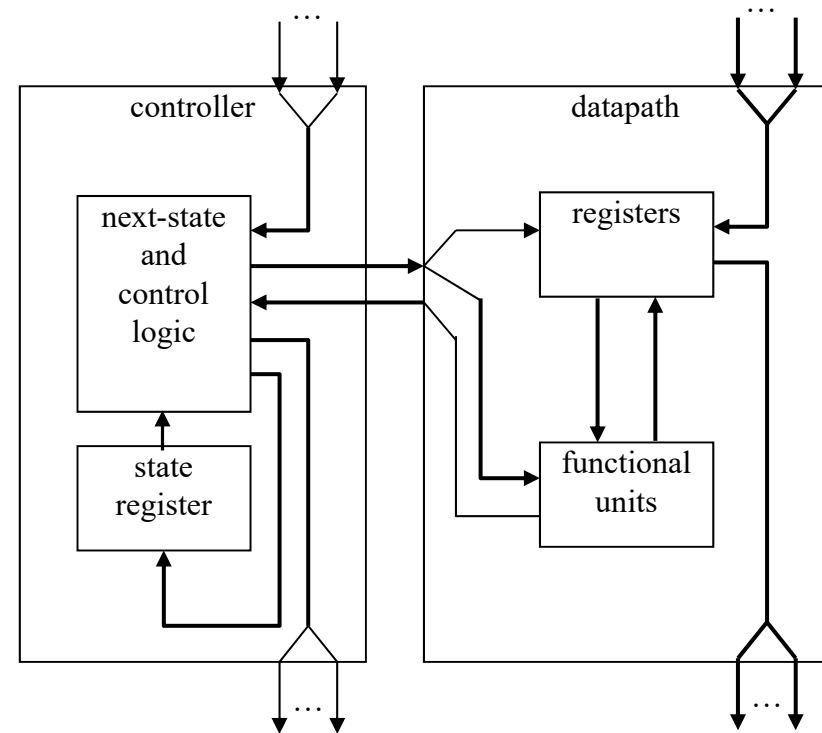
# 6. Completing the GCD custom single-purpose processor design



- We finished the datapath
- We have a state table for the next state and control logic
  - All that's left is **combinational logic design**
- This is *not* an optimized design, but we see the basic steps




a view inside the controller and datapath
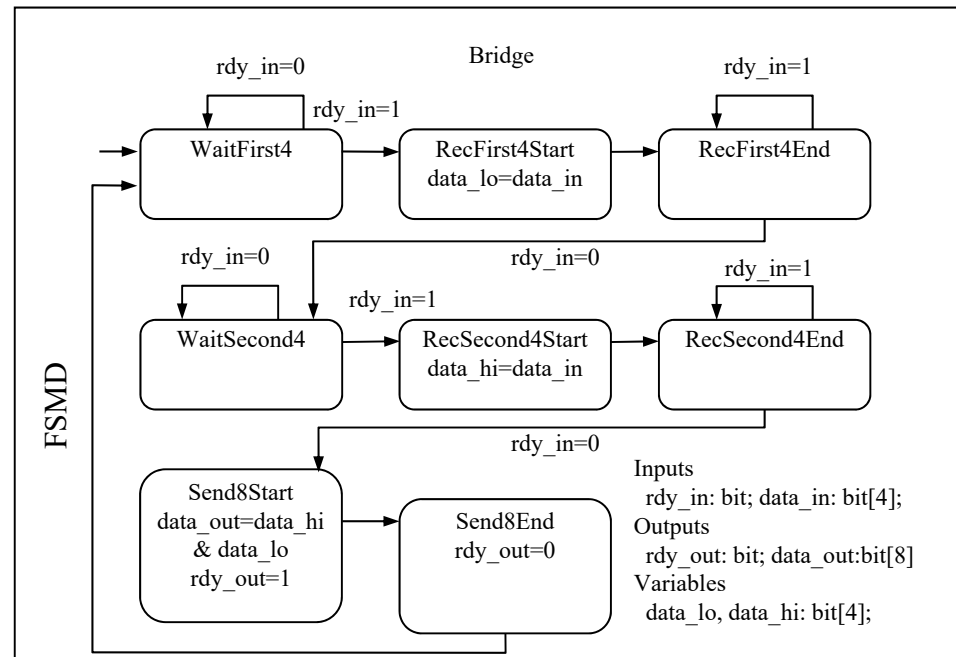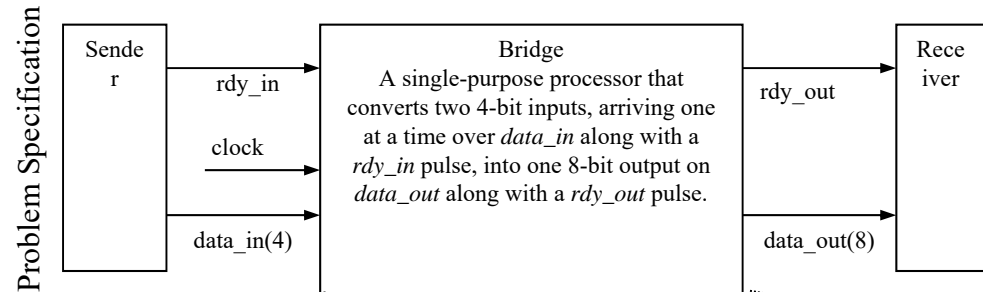
# 2.5 RT-level Custom Single-Purpose Processor Design

- We often start with a state machine, rather than program.
  - Especially when explicit cycle timing is important.
- Example
  - Bus bridge that converts 4-bit bus to 8-bit bus
  - Start with FSMD
  - Known as register-transfer (RT) level
  - Exercise: complete the design


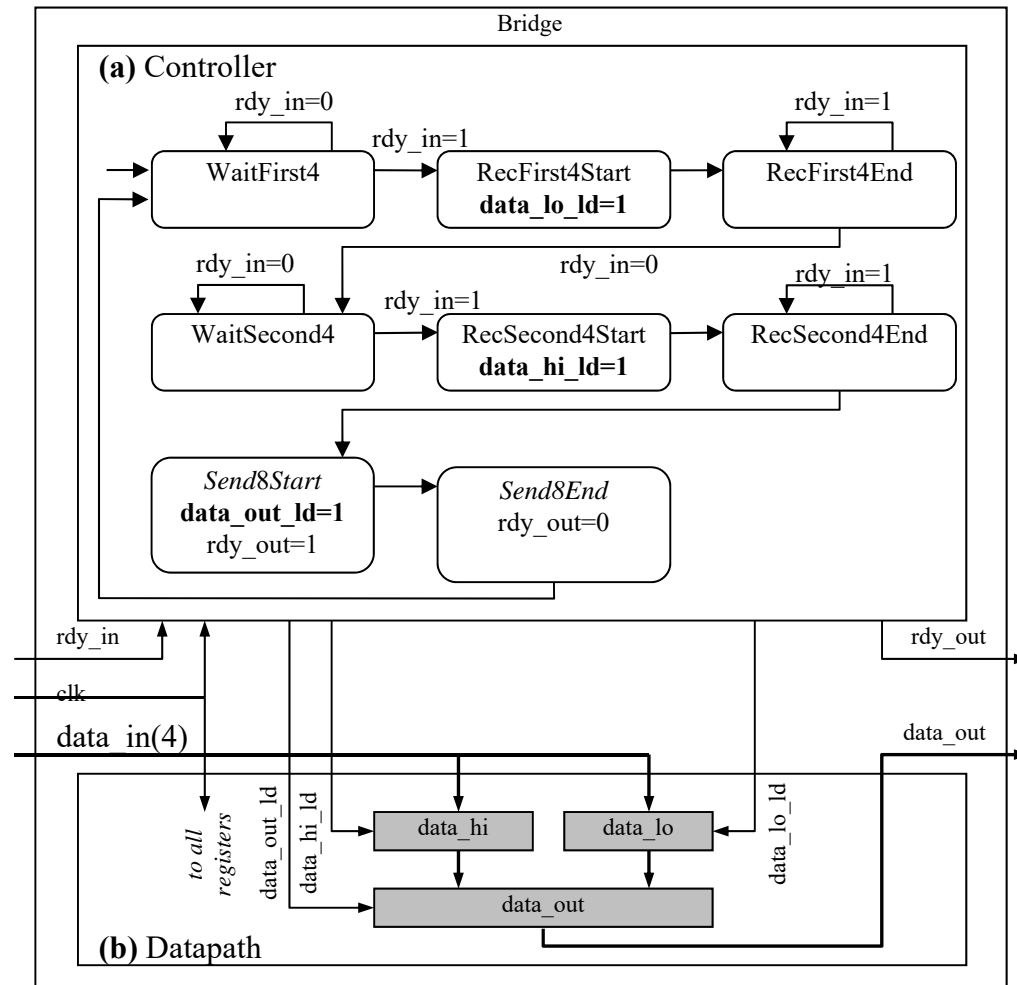
# RT-level custom single-purpose processor design (cont')



# 2.6 Optimizing Custom Single-Purpose Processors

---

- **Optimization** is the task of making design metric values the best possible.
- Optimization opportunities
  - A. Original program / algorithm
  - B. FSM
  - C. Datapath
  - D. FSM

# A. Optimizing the original program

---

- Analyze program attributes and look for areas of possible improvement
  - Time and space complexity
    - Number of computations
    - Size of variable
  - Operations used
    - Multiplication and division are very expensive.

# Optimizing the original program: Using Modulo operation

## Original program

```
0: int x, y;
1: while (1) {
2:   while (!go_i);
3:   x = x_i;
4:   y = y_i;
5:   while (x != y) {
6:     if (x < y)
7:       y = y - x;
8:     else
9:       x = x - y;
   }
9:   d_o = x;
}
```

replace the subtraction  
operation(s) with  
**modulo operation** in  
order to speed up  
program

## Optimized program

```
0: int x, y, r;
1: while (1) {
2:   while (!go_i);
   // x must be the larger
   number
3:   if (x_i >= y_i) {
4:     x=x_i;
5:     y=y_i;
   }
6:   else {
7:     x=y_i;
8:     y=x_i;
   }
9:   while (y != 0) {
10:    r = x % y;
11:    x = y;
12:    y = r;
   }
13:   d_o = x;
}
```

GCD(42, 8) - 9 iterations to complete the loop

x and y values evaluated as follows : (42, 8),  
(43, 8), (26,8), (18,8), (10, 8), (2,8), (2,6),  
(2,4), (2,2).

GCD(42,8) - 3 iterations to complete the loop

x and y values evaluated as follows: (42, 8),  
(8,2), (2,0)




# B. Optimizing the FSMD

---

- Areas of possible improvements
  - Scheduling
    - Task of assigning operations from the original program to states in an FSMD.
  - Merge states
    - States with constants on transitions can be eliminated: Transition taken is already known
    - States with independent operations can be merged
  - Separate states
    - States which require complex operations ( $a*b*c*d$ ) can be broken into smaller states to reduce hardware size


# Optimizing the FSMD (cont.)

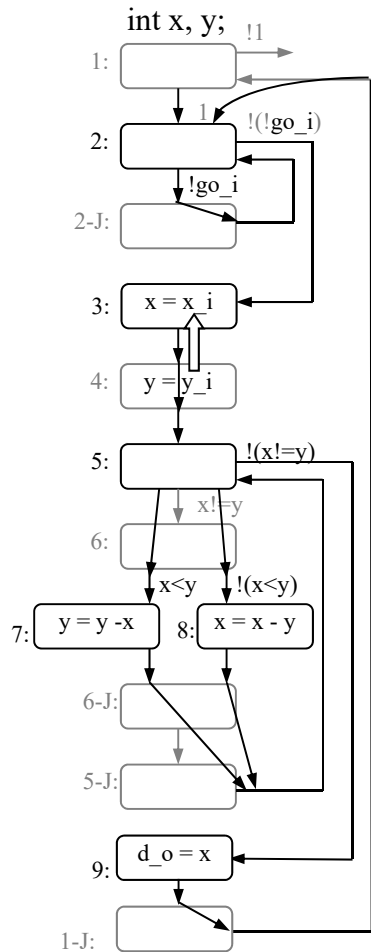

**Original FSMD**

- eliminate state 1* – transitions have constant values
- merge state 2 and state 2J* – no loop operation in between them
- merge state 3 and state 4* – assignment operations are independent of one another
- merge state 5 and state 6* – transitions from state 6 can be done in state 5
- eliminate state 5J and 6J* – transitions from each state can be done from state 7 and state 8, respectively
- eliminate state 1-J* – transition from state 1-J can be done directly from state 9

**Optimized FSMD**

 

# C. Optimizing the datapath

---

- **Sharing** of functional units
  - One-to-one mapping, as done previously, is not necessary
  - If same operation occurs in different states, they can share a single functional unit
- **Multi-functional units**
  - **ALUs** support a variety of operations, it can be shared among operations occurring in different states
- **Allocation**: Choose RT components to use
- **Bind**: Map operations from FSMD to components.

# D. Optimizing the FSM

---

- **State encoding**

- Task of assigning a unique bit pattern to each state in an FSM
- Size of state register and combinational logic vary
- Can be treated as an ordering problem

- **State minimization**

- Task of merging equivalent states into a single state
  - **State equivalent** if for all possible input combinations the two states generate the same outputs and transitions to the next same state

# Summary

---

## Custom single-purpose processors

- For non-standard tasks

## ■ Optimized Design

- Straightforward design techniques
- Can be built to execute algorithms
- Typically start with FSM/D
- CAD tools can be of great assistance.



# References

---

- [1] Frank Vahid, "Embedded system design: A unified hardware/software introduction", John Wiley & Sons, 2002.