

**EE414 Embedded Systems**

# **Ch 4. Standard Single Purpose Processors: Peripherals**

**Part 5/5: Display & Keyboard Interface**



Byung Kook Kim  
School of Electrical Engineering  
Korea Advanced Institute of Science and Technology

# Overview

---

## **Part 5/5: Display & Keyboard Interface**


- 4.31 Keyboard Interface
- 4.32 Touchscreen
- 4.33 Display Interface
- 4.34 LCD Display
- 4.35 Bit Manipulation

# 4.31 Keyboard Interface

## ■ A. Switch
 
### ■ Two-position switch

- Common device: Alone, in groups, and keyboards
- Interfacing with pull-up resistor
  - Switch open: Out = Vcc
  - Switch closed: Out = GND



### ■ Three-position switch


- Common, Normally open, Normally closed.

# Switch Debouncing

---

- **Switch bounce**

 - Just after the contact position is changed, there is a brief period during which the position of the switch is **indefinite**.
- If the contacts are coming together, they may **contact and then separate several times**.
- A switch must be **debounced** to multiple contacts caused by mechanical bouncing:



# Switch Debouncing (II)

## ■ Debouncing solution (I)

### ■ Delay

- Test the switch both before and after the delay.
  - If they disagree, the switch is moving.
  - If they agree, the switch is probably in a stable position.
- This delay is generally from 1 to about 20 ms.
  - Depending on the switch structure.
- Delay routine:


```
delay:  sub #1, R7      ; Enter with delay count in R7
        bne delay     ; Keep counting until 0
        rts           ; Return from subroutine
```

# Switch Debouncing (III)

## ■ Debouncing solution (II)


 
### ■ Hardware debouncing ->

- Set-reset flip-flop with two NOR gates
- Three-position switch
- Assume that the bounces are not so terrible that the switch recontacts the side it already has left.



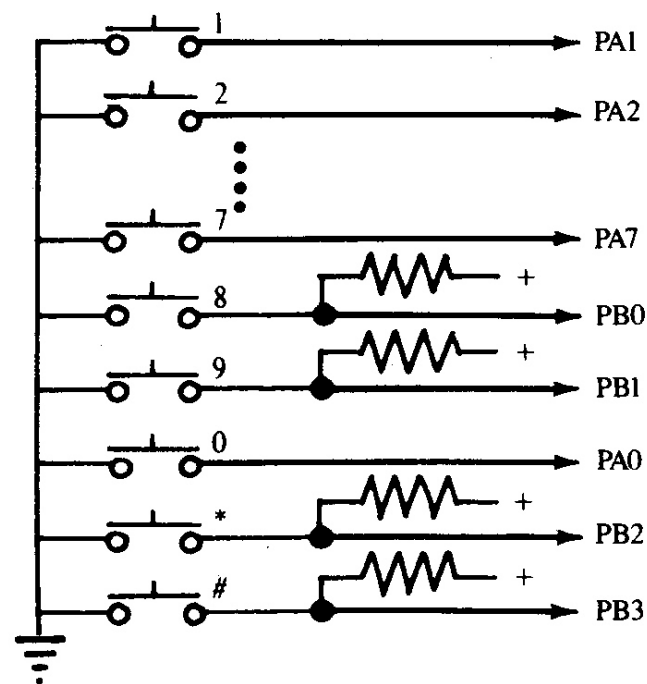 
## B. Telephone Keyboard

- **Standard telephone pushbutton keyboard** →
  - 12 buttons: 0 – 9, \*, #
  - 12 parallel input bits are required.


 
# C. Telephone Keyboard Grid

- **Reduce wires:**  $m*n$  switches using only  $m+n$  wires
  - 12 switches with  $4+3=7$  wires
  - 80 switches with  $10+8=18$  or  $9+9=18$  wires!





# Program for Keyboard Grid

## ■ Notes

- Read one column at a time
  - Force vertical line to be low & read horizontal lines.

## ■ Algorithm

- Make  $PA2-0 = 011$
- Read horizontal lines. If there is a zero, a key is down in this column.
- If not,  $PA2-0 = 101$ . If there is a zero, a key is down in this column.
- If not,  $PA2-0 = 110$ . If there is a zero, a key is down in this column.
- *Debouncing*: If a key is found down, save the code, delay, and repeat the reading process.
- *False Key*: If the newly-read code does not match the old code, save the new code as the old code and go back to Step 1 for another try.
- If the newly-read code does match the old code, go on to **search table** for the value of the key.

# Program for Keyboard Grid (II)

- Codes for the keyboard grid (Search table)

Key	PA6 - 0	Hex
0	0 1 1 1 1 0 1	3D
1	1 1 1 0 1 1 0	76
2	1 1 1 0 1 0 1	75
3	1 1 1 0 0 1 1	73
4	1 1 0 1 1 1 0	6E
5	1 1 0 1 1 0 1	6D
6	1 1 0 1 0 1 1	6B
7	1 0 1 1 1 1 0	5E
8	1 0 1 1 1 0 1	5D
9	1 0 1 1 0 1 1	5B
*	0 1 1 1 1 1 0	3E
#	0 1 1 1 0 1 1	3B


# Bidirectional Keyboard Grid Algorithm

## ■ Advantages


- Only two read operations without column scanning
 
## ■ Algorithm

- Make PA2-0 output and PA6-3 as input
- Force PA2-0 low and read to x.
- Make PA6-3 output and PA2-0 input
- Force PA6-3 low and read to y.
- Combine x and y into one byte. The result is the same code as the table in slide 9.



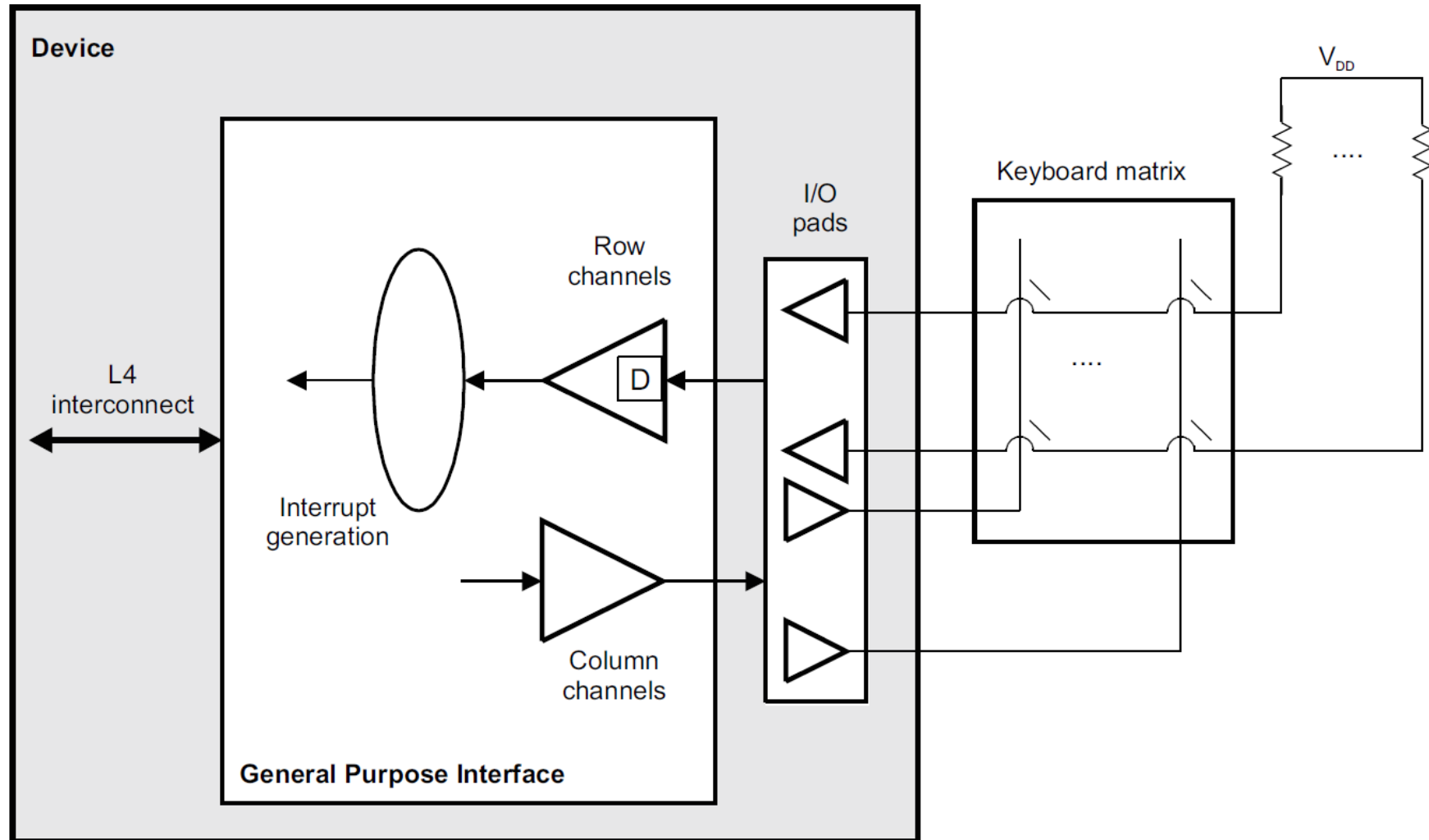
# General-Purpose Interface Used as a Keyboard Interface



 
# 4.32 Touchscreen

---

- Includes input and output device.
- Input device is a **two-dimensional voltmeter**:




# Touchscreen Position Sensing

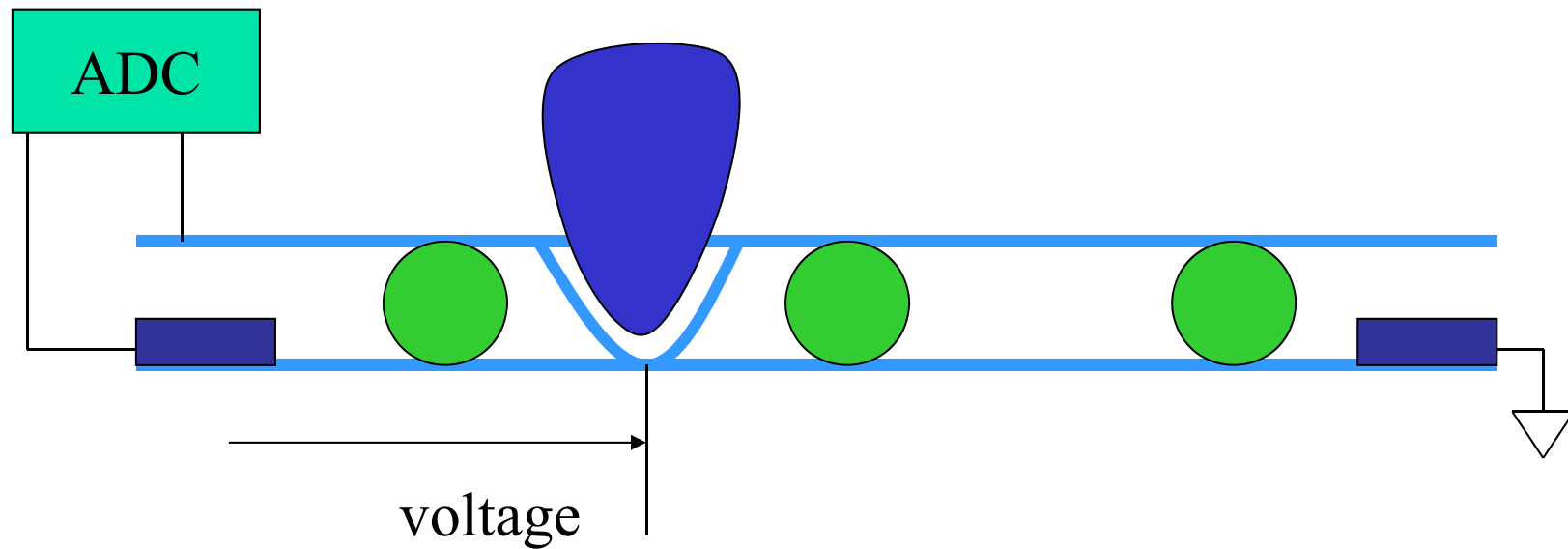

# 4.33 Display Interface

 
- **A. Display of digits**

- Seven-segment display →
- 16-segment display
- Array of dots →




- **Types**

- Common anode →
- Common cathode

 
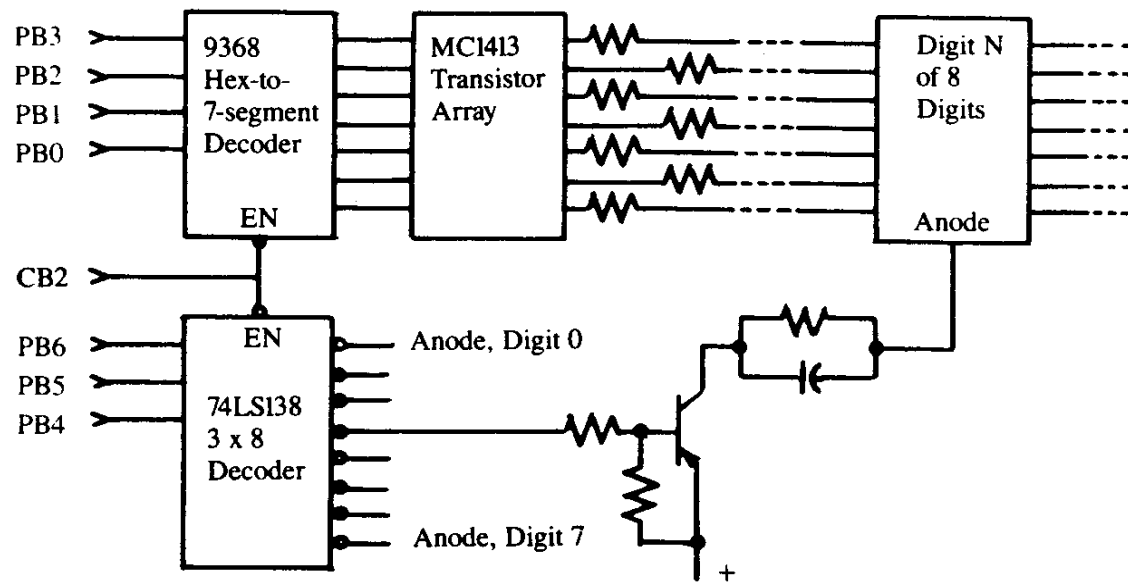
# Display Interface (II)

- Multiple-digit seven-segment display
  - Ex: 8 digits →
    - $7 \times 8 = 56$  wires
    - $7 + 8 = 15$  wires
    - $4 + 3 = 7$  wires





# Display Interface (III)

## ■ Algorithm

```
Given c[i], i=0, 1, ..., 7
For digit d=0, 1, ..., 7
    Output digit selection d
    Turn on: Output 7-segment display c[d]
    Delay
    Turn off 7-segment display
End of d
```


## ■ Ghost elimination

- Place turn-on and turn-off side by side after the move
  - (Include red lines as above).

# Display Interface (IV)
 
## ■ Driver ICs - ULN2803

- **8-bit 50V 500mA TTL-input NPN darlington drivers.**
- The drivers need **no power supply**; the VDD pin is the common cathode of the eight integrated protection diodes.
- The eight NPN Darlington connected transistors in this family of arrays are ideally suited for interfacing between low logic level digital circuitry (such as TTL, CMOS or PMOS/NMOS) and the higher current/voltage requirements of lamps, relays, printer hammers or other similar loads for a broad range of computer, industrial, and consumer applications.
- All devices feature **open-collector outputs** and **free wheeling clamp diodes** for transient suppression.




# Display Interface (V)

## ■ Driver ICs – uDN2981
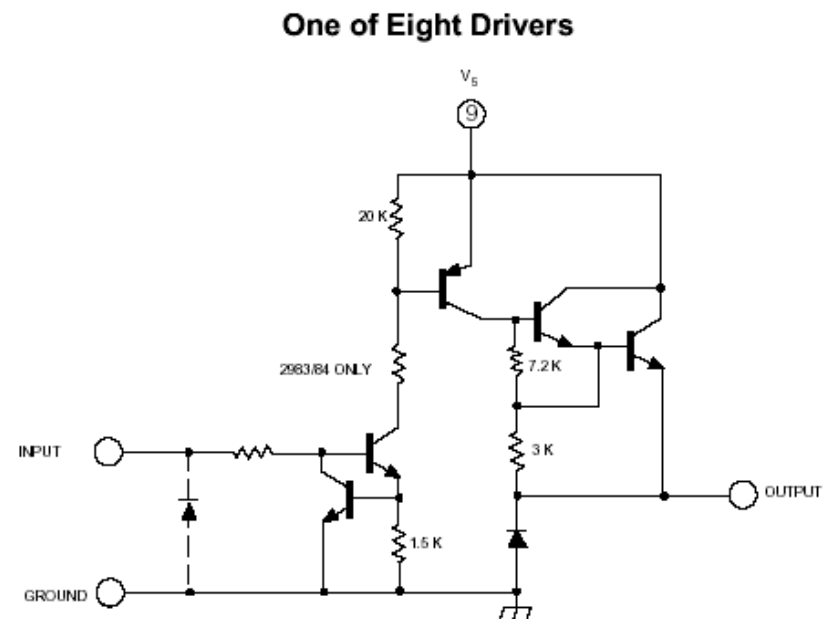
### ■ **8-CHANNEL SOURCE DRIVERS**

- Recommended for high-side switching applications that benefit from separate logic and load grounds, these devices encompass load supply voltages to 80 V and output currents to **-500 mA**.
- These 8-channel source drivers are useful for interfacing between low-level logic and high-current loads.
- Typical loads include relays, solenoids, lamps, stepper and/or servo motors, print hammers, and LEDs.




# Display Interface (VI)


- **B. Dot matrix display**
  - English 1 x 20 characters
    - 7 x 100 dot matrix display
  - Korean 1 x 20 characters
    - 16 x 320 dot matrix display



A.LTP-2057A

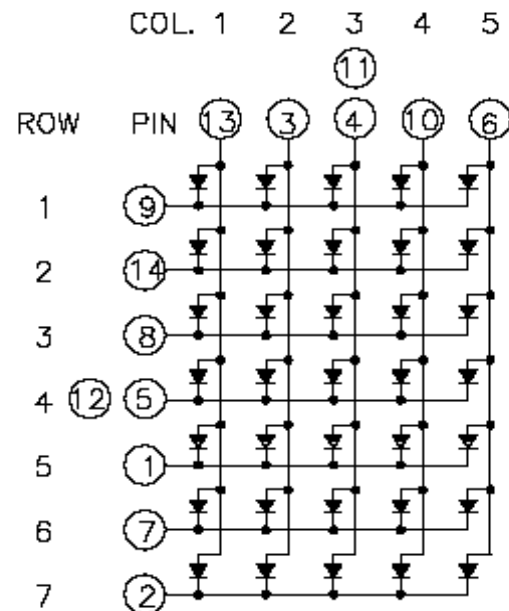

B.LTP-2157A

 


# Display Interface (VII)

---
 
## ■ C. Color display

- Red & Green LED: red, green, yellow
- Color LED: red, green, blue LEDs
- 1024 x 768 True color
  - 1024 x 768 x 3 bytes for RGB



# 4.34 LCD Display

---

- **LCD (liquid crystal display)**
  - Advantages
    - Thinner and lighter
    - Draw much less power than cathode ray tubes (CRTs)
  - LCD History
    - Liquid crystals were first discovered in 1888, by Austrian botanist **Friedrich Reinitzer**.
    - Reinitzer observed that when he melted a curious cholesterol-like substance (**cholesteryl benzoate**), it first became a cloudy liquid and then cleared up as its temperature rose.
    - Upon cooling, the liquid turned blue before finally crystallizing.
    - Eighty years passed before **RCA** made the first experimental LCD in 1968.

# LCD Display (II)

---

## ■ Principles on LCD

- Liquid crystals are closer to a liquid state than a solid.
  - It takes a fair amount of heat to change a suitable substance from a solid into a liquid crystal, and it only takes a little more heat to turn that same liquid crystal into a real liquid.
  - Very sensitive to **temperature**: used to make thermometers and mood rings.
- Depending on the temperature and particular nature of a substance, liquid crystals can be in one of several distinct phases.
  - **Nematic phase**: Affected by **electric current**.
  - A particular sort of nematic liquid crystal, called **twisted nematics (TN)**, is naturally twisted.
  - Applying an electric current to these liquid crystals will untwist them to varying degrees, depending on the current's voltage.

# LCD Display (III)

---

- **LCD Systems**

- **Common-plane-based LCDs**

- Good for simple displays that need to show the same information over and over again.
    - Watches and microwave timers

- **Passive-matrix LCDs (TN, STN LCDs)**

- Use a simple grid to supply the charge to a particular pixel on the display.
    - **Slow response time and imprecise voltage control.**

- **Active-matrix LCDs**



- Depend on matrix of **thin film transistors (TFT)**: tiny switching transistors and capacitors.
    - To address a particular pixel, the proper row is switched on, and then a charge is sent down the correct column: **gray scale**.
    - Most displays today offer 256 levels of brightness per pixel.




# LCD Display (IV)
  
## ■ LCD Color

- Must have **three subpixels** with red, green and blue color filters to create each color pixel.
- Through the careful control and variation of the voltage applied, the intensity of each subpixel can range over **256 shades**.
- Combining the subpixels produces a possible palette of **16.8 million colors** (256 shades of red x 256 shades of green x 256 shades of blue).
- Enormous number of transistors.
  - Ex: A typical laptop computer supports resolutions up to 1,024x768.
  - 1,024 columns by 768 rows by 3 subpixels, we get 2,359,296 transistors etched onto the glass!
  - If there is a problem with any of these transistors, it creates a "bad pixel" on the display.



# LCD Controller

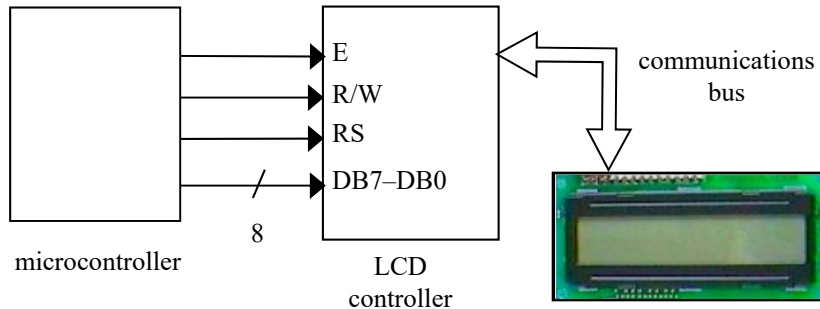

```
void WriteChar(char c){
    RS = 1;           /* indicate data being sent */
    DATA_BUS = c;    /* send data to LCD */
    EnableLCD(45);    /* toggle the LCD with appropriate delay */
}
```

CODES	
I/D = 1 cursor moves left	DL = 1 8-bit
I/D = 0 cursor moves right	DL = 0 4-bit
S = 1 with display shift	N = 1 2 rows
S/C = 1 display shift	N = 0 1 row
S/C = 0 cursor movement	F = 1 5x10 dots
R/L = 1 shift to right	F = 0 5x7 dots
R/L = 0 shift to left	

RS	R/W	DB <sub>7</sub>	DB <sub>6</sub>	DB <sub>5</sub>	DB <sub>4</sub>	DB <sub>3</sub>	DB <sub>2</sub>	DB <sub>1</sub>	DB <sub>0</sub>	Description	
0	0	0	0	0	0	0	0	0	1	Clears all display, return cursor home	
0	0	0	0	0	0	0	0	1	*	Returns cursor home	
0	0	0	0	0	0	0	1	I/D	S	Sets cursor move direction and/or specifies not to shift display	
0	0	0	0	0	0	1	D	C	B	ON/OFF of all display(D), cursor ON/OFF (C), and blink position (B)	
0	0	0	0	0	1	S/C	R/L	*	*	Move cursor and shifts display	
0	0	0	0	1	DL	N	F	*	*	Sets interface data length, number of display lines, and character font	
1	0	WRITE DATA									Writes Data

# 4.35 Bit Manipulation

- Changing i-th bit
  - `var = var EOR (1 << i);`
- Clear lower half-byte
  - `var = var & 0xf0;`
- Combine bit groups
  - `var = (x & 0xff00) | (y & 0xff);`
- Swap half-bytes
  - `ROL.B #4, R0`
- Binary to BCD (2 digits)
  - `Bcd = ((bin/10)<<4) | (bin%10);`
- BCD to binary (2 digits)
  - `Bin = (bcd>>4)*10 + (bcd&0x0f);`

# References

---

- Keyboard interface, display interface, and bit manipulation
  - William Eccles, "Microprocessor systems – A 16-bit approach", Addison Wesley, 1985.
- Display interface & LCD display
  - Search Internet

